


HY220

Using, Modeling and Implementing FSMs




Review: What's an FSM?

- ❑ Next state is function of state and input

 - ❑ Moore Machine: output is a function of the state



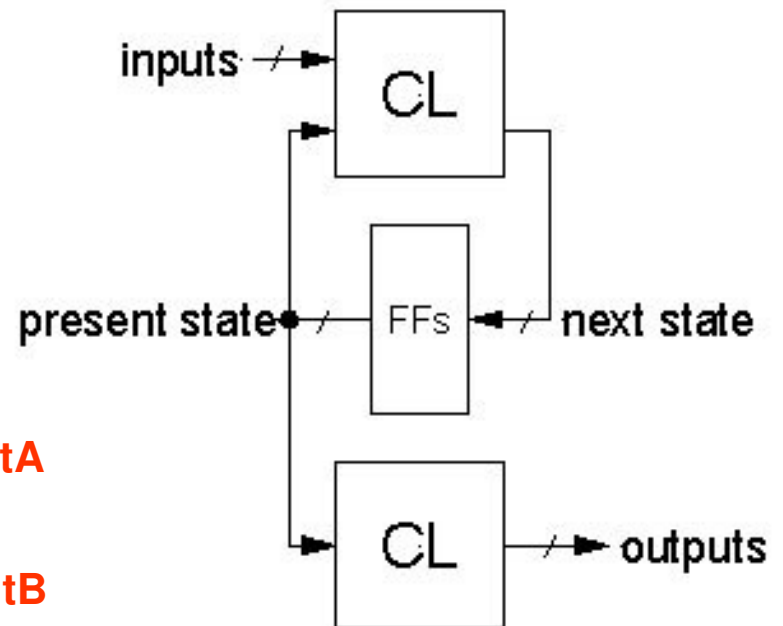  - ❑ Mealy Machine: output is a function of state and input




Review: Formal Design Process

- ❑ **Review of Design Steps:**
 - 1. Circuit functional specification**
 - 2. State Transition Diagram**
 - 3. Symbolic State Transition Table**
 - 4. Encoded State Transition Table**
 - 5. Derive Logic Equations**
 - 6. Circuit Diagram**
 - FFs for state**
 - CL for NS and OUT**

Finite State Machine Representations

 - ❑ **States:** determined by possible values in sequential storage elements
- ❑ **Transitions:** change of state
- ❑ **Clock:** controls when state can change by controlling storage elements




- ❑ **Sequential Logic**
 - ◆ Sequences through a series of states
 - ◆ Based on sequence of values on input signals
 - ◆ Clock period defines elements of sequence

How do I use FSMs ?


Block

Control logic (FSM)

 

Control signals

Datapath (registers, muxes, adders...)

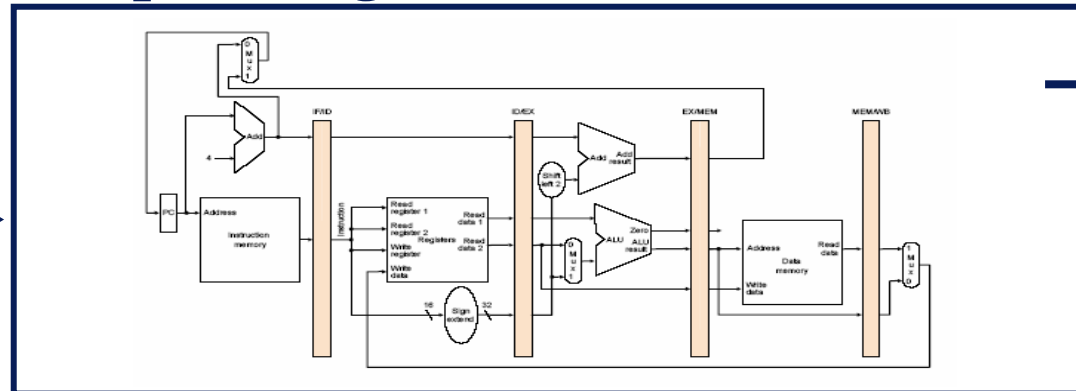


External
Outputs

Example1 : Reduce 1s example

□ Change the first 1 to 0 in each string of 1's


◆ Example Moore machine implementation
 
```
module Reduce(Out, Clock, Reset, In);  
    output Out;  
    input Clock, Reset, In;  
  
    reg Out;  
    reg [1:0] CurrentState; // state register  
    reg [1:0] NextState;  
  
    // State assignment  
    localparam STATE_Zero = 2'h0,  
                STATE_One1 = 2'h1,  
                STATE_Two1s = 2'h2,  
                STATE_X = 2'hX;
```



Moore Verilog FSM: combinational part

```
always @(In or CurrentState) begin
    NextState = CurrentState;
    Out = 1'b0;
    case (CurrentState)
        STATE_Zero: begin // last input was a zero
            if (In) NextState = STATE_One1;
        end
        STATE_One1: begin // we've seen one 1
            if (In) NextState = STATE_Two1s;
            else NextState = STATE_Zero;
        end
        STATE_Two1s: begin // we've seen at least 2 ones
            Out = 1;
            if (~In) NextState = STATE_Zero;
        end
        default: begin // in case we reach a bad state
            Out = 1'bx;
            NextState = STATE_X;
        end
    endcase
end
```

 


include all signals
that are input to state
and output equations

Moore Verilog FSM: state part

```
// Implement the state register
always @ (posedge Clock) begin
    if (Reset) CurrentState <= STATE_Zero;
    else CurrentState <= NextState;
end
endmodule
```

 Note: posedge Clock requires NONBLOCKING ASSIGNMENT.



Blocking Assignment <-> Combinational Logic

Nonblocking Assignment <-> Sequential Logic (Registers)

Mealy Verilog FSM for Reduce-1s example

```


module Reduce(Clock, Reset, In, Out);
    input    Clock, Reset, In;
    output   Out;
    reg      Out;
    reg      CurrentState;          // state register
    reg      NextState;

    localparam STATE_Zero = 1'b0,
                STATE_One = 1'b1;

    always @(posedge Clock) begin
        if (Reset) CurrentState <= STATE_Zero;
        else CurrentState <= NextState;
    end

    always @ (In or CurrentState) begin
        NextState = CurrentState;
        Out = 1'b0;
        case (CurrentState)
            State_Zero: if (In) NextState = STATE_One;
            State_One: begin // we've seen one 1
                if (In) NextState = STATE_One;
                else NextState = STATE_Zero;
                Out = In;
            end
        endcase
    end
endmodule


```

 


Note: smaller state machine

Output = G(state, input)

Moore vs Mealy

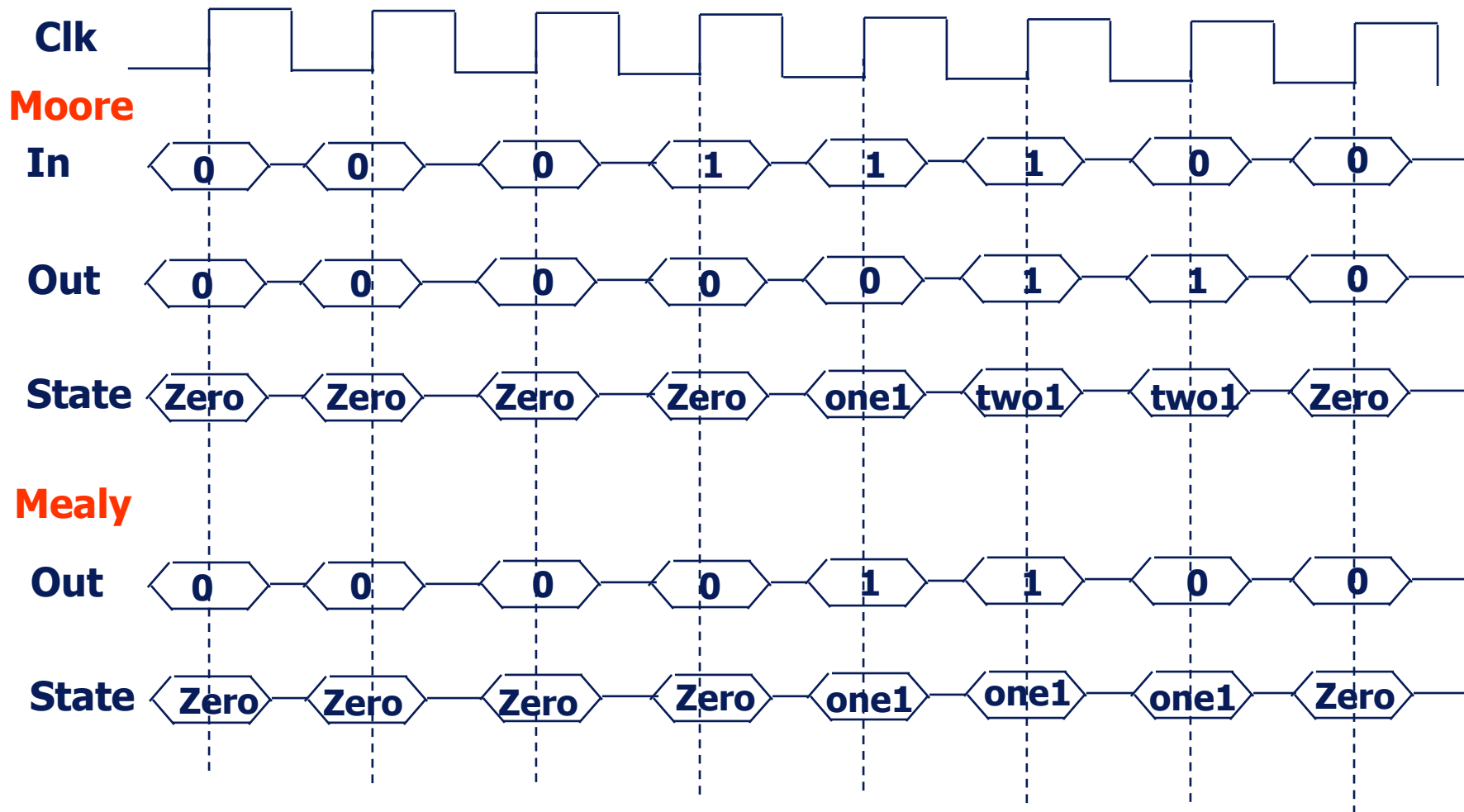

Example2: Transition Diagram

 

FSM 1/4 : CL

```
module fsmM(ReceiveSt, ErrorSt, Start,
            Stop, Error, Clk, Reset_);
//
input  Start, Stop, Error, Clk, Reset_;
output ReceiveSt, ErrorSt;
//
parameter [1:0] IdleState    = 0,
               ReceiveState = 1,
               ErrorState    = 3;
//
reg [1:0] FSMstate, nxtFSMstate;
//
always @(FSMstate or Start or Stop or Error) begin
//
    case (FSMstate)
```

FSM 2/4 : CL

IdleState:

```
begin
  if(Error) nxtFSMstate <= ErrorState;
  else begin
    if(Start) nxtFSMstate <= ReceiveState;
    else nxtFSMstate <= IdleState;
  end
end
```

//

ReceiveState:

```
begin
  if(Error) nxtFSMstate <= ErrorState;
  else begin
    if(Stop) nxtFSMstate <= IdleState;
    else nxtFSMstate <= ReceiveState;
  end
end
```

FSM 3/4: register

```
ErrorState : nxtFSMstate <= IdleState;
default    : nxtFSMstate <= IdleState;
endcase
end

always @(posedge Clk) begin
    if (Reset) FSMstate <= #`dh IdleState;
    else FSMstate <= #`dh nxtFSMstate;
End
```

Mealy FSM 4/4 : outputs

```
reg ReceiveSt;  
wire SetRcvSt = (FSMstate==IdleState)&Start;  
wire ClrRcvSt = (FSMstate==ReceiveState)&(Error|Stop);  
//  
always @(posedge Clk) begin  
    if (~Reset_) ReceiveSt <= 0;  
    else ReceiveSt <= (ReceiveSt | SetRcvSt)&~ClrRcvSt;  
end  
//  
wire ErrorSt = FSMstate[1];  
//  
endmodule
```

Output “ReveiveSt” depends
on inputs.